

# Design of VLSI Integrated Circuits

*A (very) deep dive into computing machines...*

Olivier Sentieys

Inria

Univ. Rennes, Irisa

olivier.sentieys@inria.fr



<http://people.rennes.inria.fr/Olivier.Sentieys>

# Cairn Team at a Glance

Inria Rennes




Enssat Lannion

- *Energy-Efficient Computing Architectures*


- IRISA/INRIA
- ~35 people, Rennes and Lannion campuses
- from INRIA, Univ. Rennes 1, ENS Rennes
- **Electrical Engineering & Computer Science**
- **Domain-specific** computing architectures
- Design tools and compilers

# VLSI Integrated Circuit Design

- Chips, logic gates and transistors

 


Intel's Xeon Chip

 

```
#pragma hls_design top
void my_design (int *a, int *o) {
    static int i,j;
    for(i=1;i<=n-1; i++)
    for(j=1;j<=n-1; j++)
        a[i][j] = (a[i-1][j]+a[i][j]+a[i][j-1])/3.0;
}
```

```
end if;
end process;
```

 

# Key Questions

- A deep dive into processors... *(I hope not too deep)*
- What is **CMOS**? How basic logic **gates**, registers and memory are designed?
- How to calculate the delay and the maximal **frequency**?
- How much **power** does my processor consume?
- What can advanced semiconductor **technology** bring?
- Are (homogeneous) multicores the right solution for performance or energy efficiency?
- Specializing the computer: **reconfigurable** computing




# Outline




- **The Fundamental Element: MOSFET Transistor**
- Design of CMOS Cells: Combinatorial Logic
- Memory Cells
- Delay
- Power Consumption
- Synchronous Design
- Multicore: power and utilization walls
- Hardware accelerators

# Fundamental Building Block: MOSFET Transistor

Now several billions of transistors

 


Intel's Xeon Chip

   

MOSFET: Metal Oxide Silicon Field Effect

# The Basic Element: Transistor


- Transistor as a switch

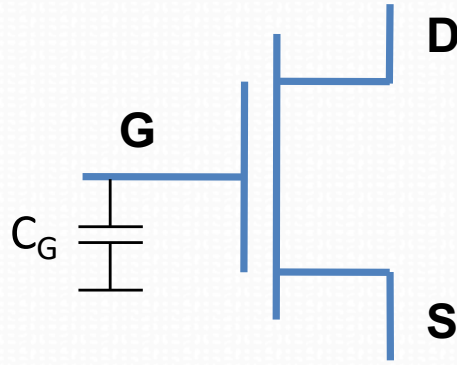

- $V_{gs} > V_t$ : NMOS on
  - Resistance  $R_{DS}$




 - $V_{gs} < V_t$ : NMOS off
  - Leakage  $I_{off}$



- Gate: capacitance  $C_G$
- Switch: resistance  $R_{DS}$

# MOS Transistor Models

 



- $W$ : gate width
- $L$ : gate length
- $t_{ox}$ : oxide width (#L/10)
- $K = \mu \cdot \epsilon \cdot W / (t_{ox} \cdot L) = k W/L$
- $\mu$ : charge-carrier effective mobility  
 NMOS (electrons)  $\mu_N = 500 \text{ cm}^2/\text{V-sec}$  #  $2 \mu\text{P}$   
 PMOS (holes)  $\mu_p = 270 \text{ cm}^2/\text{V-sec}$
- $\epsilon$ : oxide permittivity #  $4 \epsilon_0 = 3.5 \cdot 10^{-13} \text{ F/cm}$

$$I_{ds} = \begin{cases} 0 & \text{off} & V_{gs} - V_{th} < 0 \\ K \left[ (V_{gs} - V_{th})V_{ds} - \frac{V_{ds}^2}{2} \right] & \text{linear} & 0 < V_{ds} < V_{gs} - V_{th} \\ \frac{K}{2}(V_{gs} - V_{th})^2 & \text{saturated} & 0 < V_{gs} - V_{th} < V_{ds} \end{cases}$$



- $K$  defines transistor speed,  $K \propto W/L$ ,  $K_{NMOS} \sim 2 \cdot K_{PMOS}$
- Temperature increases  $\rightarrow \mu$  decreases

# Transistors Nowadays

- Intel FinFET: transistors go 3D

  

  - Fully Depleted SOI<sup>1</sup>
  - Low-power



<sup>1</sup>Silicon on Insulator



# Outline

- The Fundamental Element: MOSFET Transistor
- Design of CMOS Cells: Combinatorial Logic
- Memory Cells
- Delay
- Power Consumption
- Synchronous Design
- Multicore: power and utilization walls
- Hardware accelerators


# NMOS/PMOS Transistors

- NMOS
  - A '0' is well transmitted
  - A degraded '1' is transmitted ( $V_{dd} - V_{tn}$ )

- $V_{gs} < V_{tn}$




- $V_{gs} > V_{tn}$

 


- PMOS
  - A '1' is well transmitted
  - A degraded '0' is transmitted ( $V_{ss} + |V_{tp}|$ )

- $V_{gs} < |V_{tp}|$

 



- $V_{gs} > |V_{tp}|$

 

# Combinatorial Logic Cells


- Complementary Logic (CMOS)

CMOS Inverter

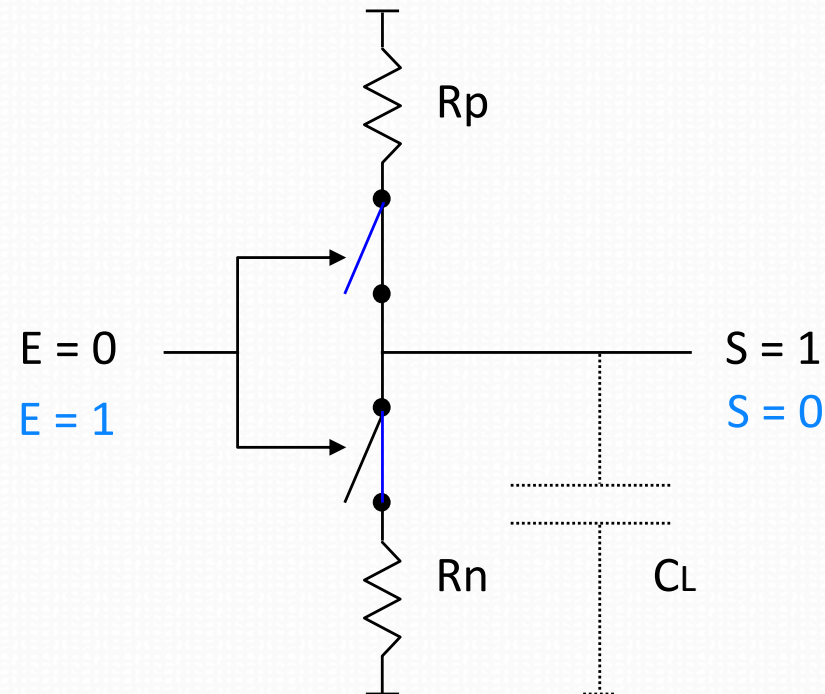 


# NAND and NOR


**NAND**

 


A	B	S
0	0	1
0	1	1
1	0	1
1	1	0

 

**NOR**

 


A	B	S
0	0	1
0	1	0
1	0	0
1	1	0

 


# Layout Design


## Transistor Schematic

 

## Layout

 


## Silicon

 


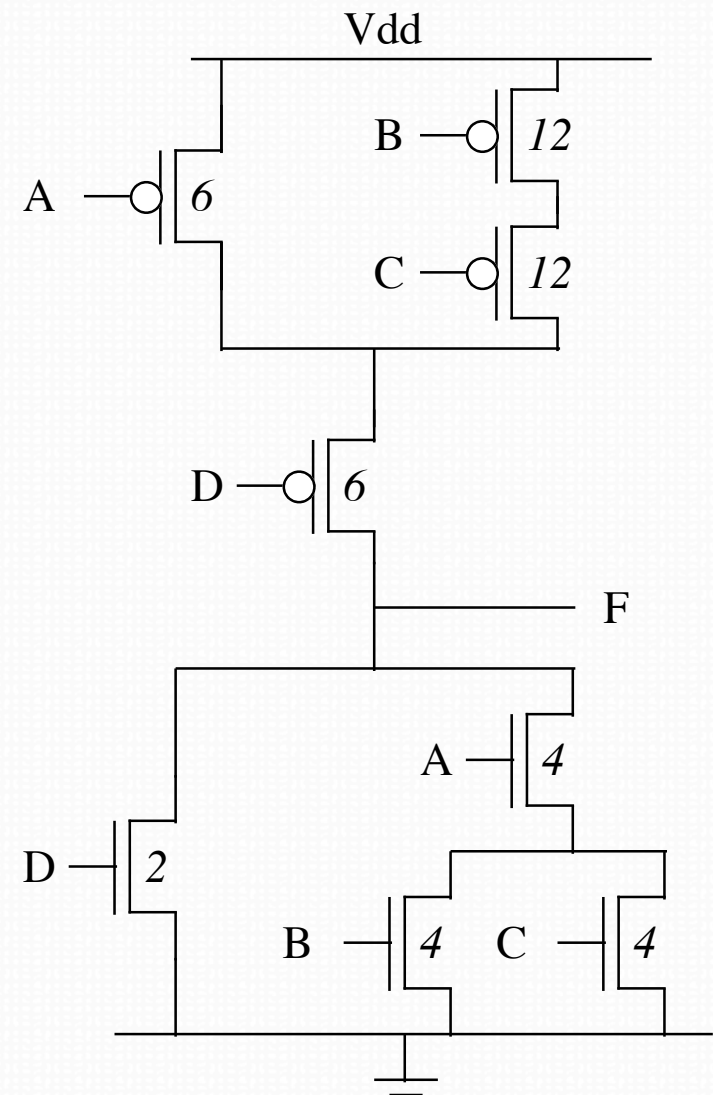
# Complex Gates



- $F = \overline{A \cdot (B + C) + D}$
- Multiple-Stage Complex Functions
  - Optimisation of the logic equation
  - Trade-off between speed and area
  - A.B.C.D
  - !A.B+A.!B (XOR)



# Complex Gates: Full Adder


- Full Adder

Ai	Bi	Ci	Co	Si
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

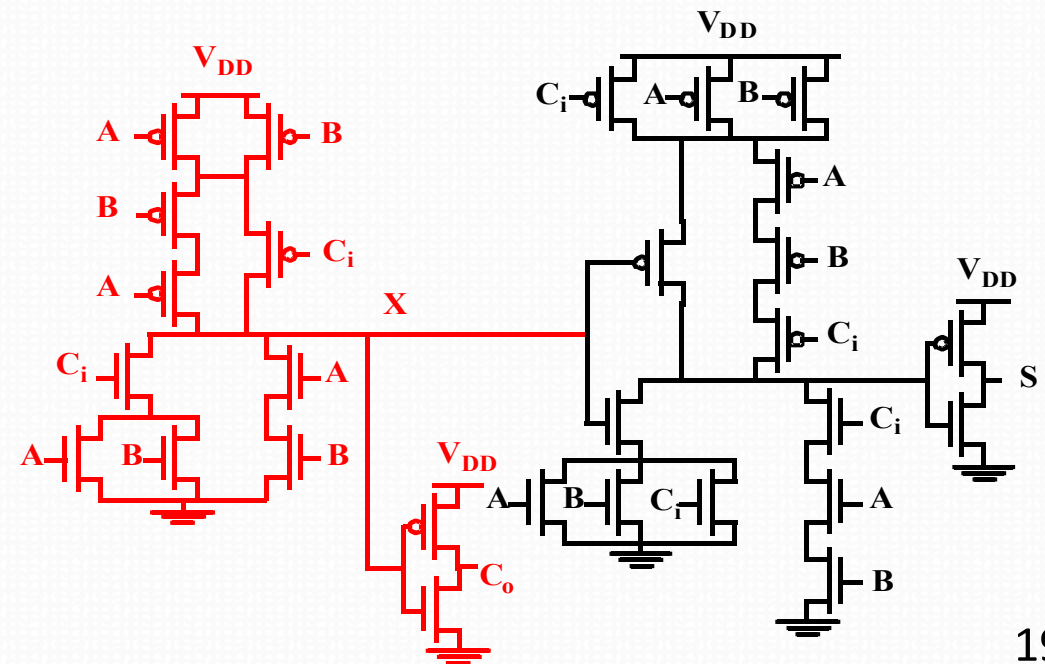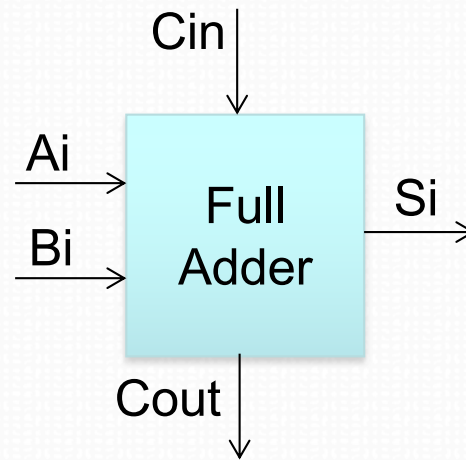


# Complex Functions

- 16-bit Adder (integer)

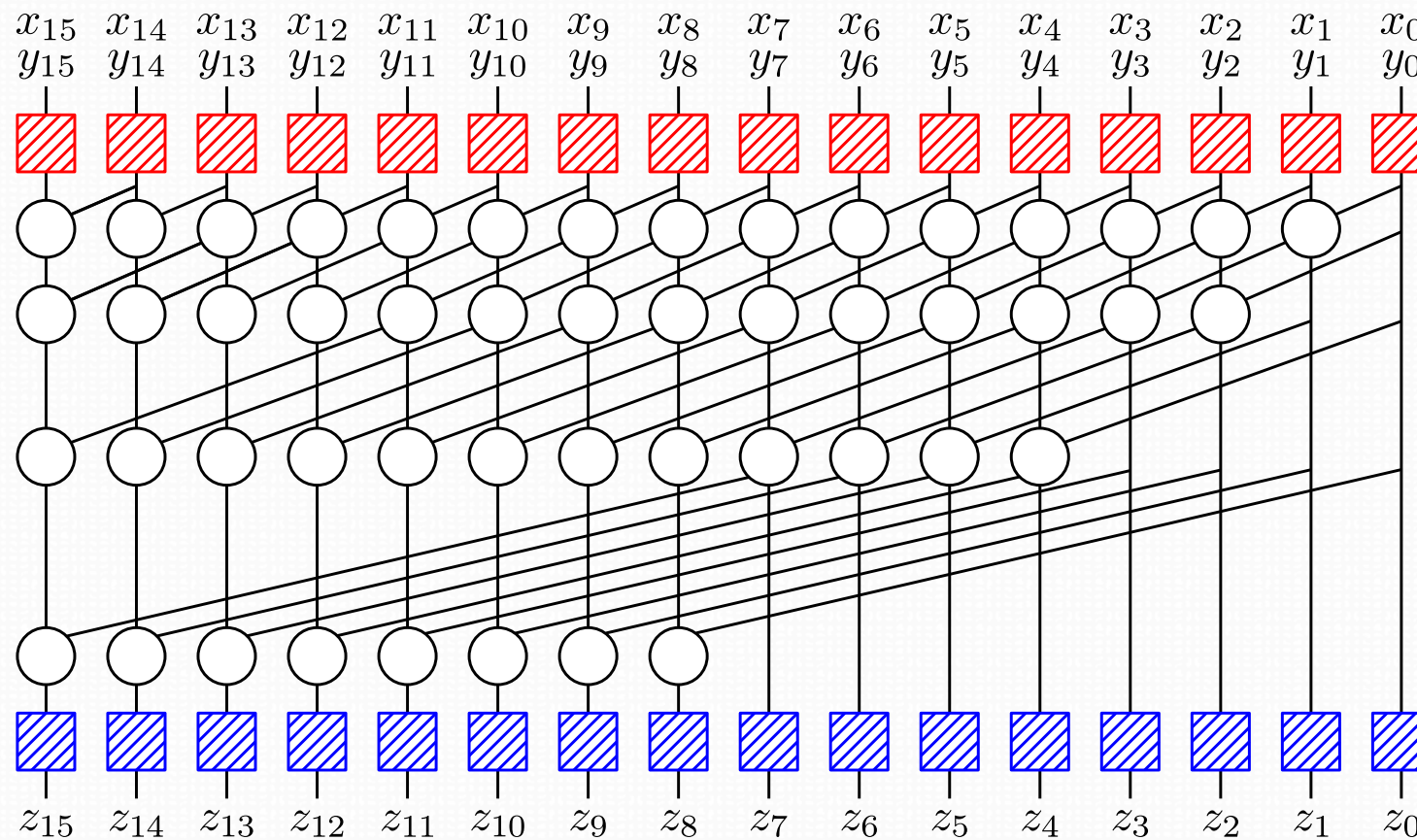

# Pass-Transistor Logic

- Switch or Transmission Gate

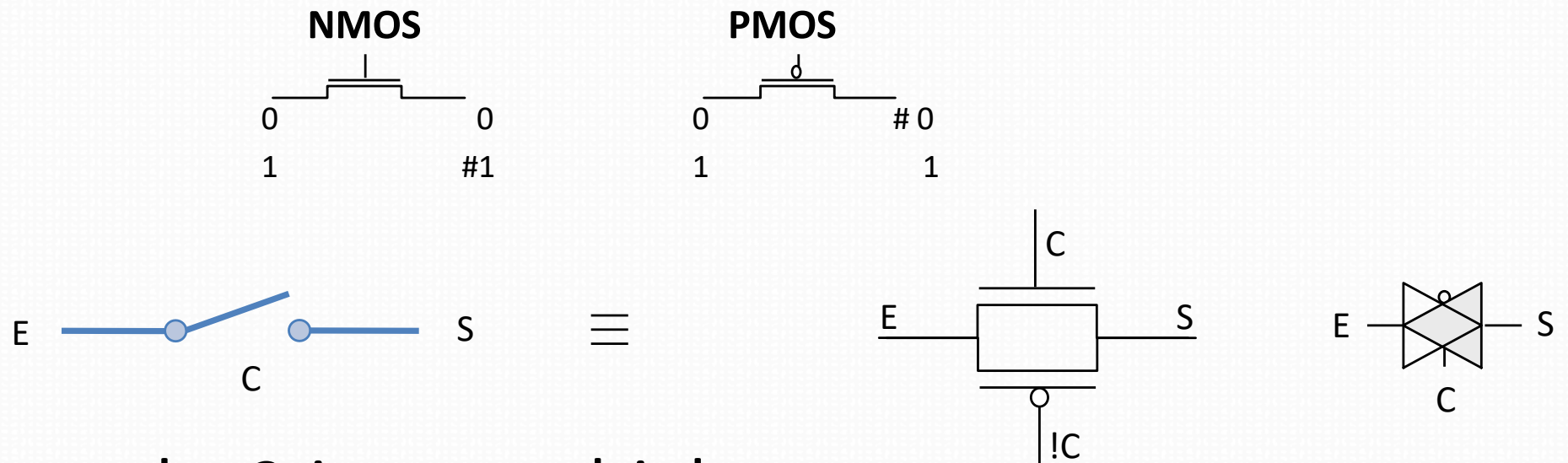

- Example: 2-input multiplexer



- Example: XOR


# Outline

- The Fundamental Element: MOSFET Transistor
- Design of CMOS Cells: Combinatorial Logic
- **Memory Cells**
- Delay
- Power Consumption
- Synchronous Design
- Multicore: power and utilization walls
- Hardware accelerators





# Storing Values


## Capacitor (dynamic) (DRAM)

 


## Latch (static) (SRAM)

 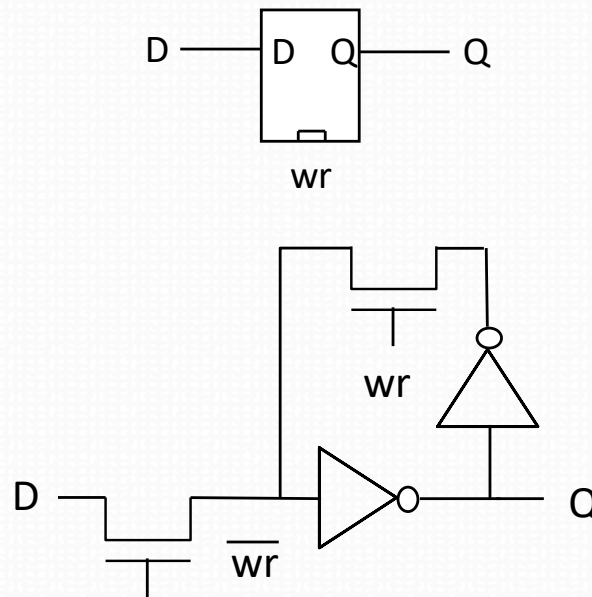

## Flip-Flop (static) (Register)


 


 - Setup Time:  $T_{setup}$
- Hold Time:  $T_{hold}$
- Propagation Time:  $T_p$



# D Flip-Flop (edge-triggered)




- Two latches in series

 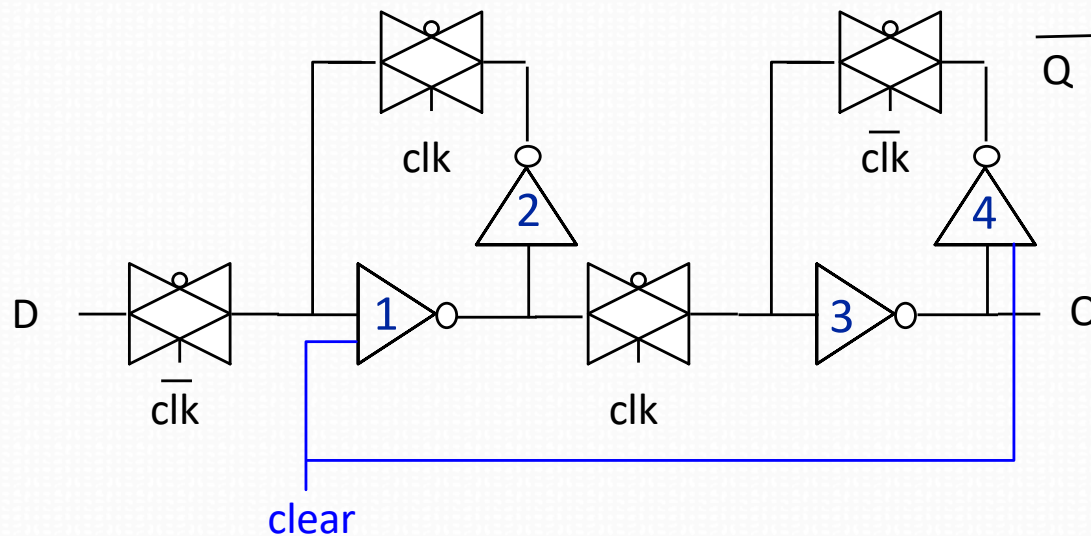

- D is sampled in inverter (1) when  $\text{clk} = 0$
- Latch (1) and (2) keeps D value when  $\text{clk} = 1$  until !D is transferred to second latch (3) and (4)
- Asynchronous clear signal: replace inv. (1) and (4) by NAND
  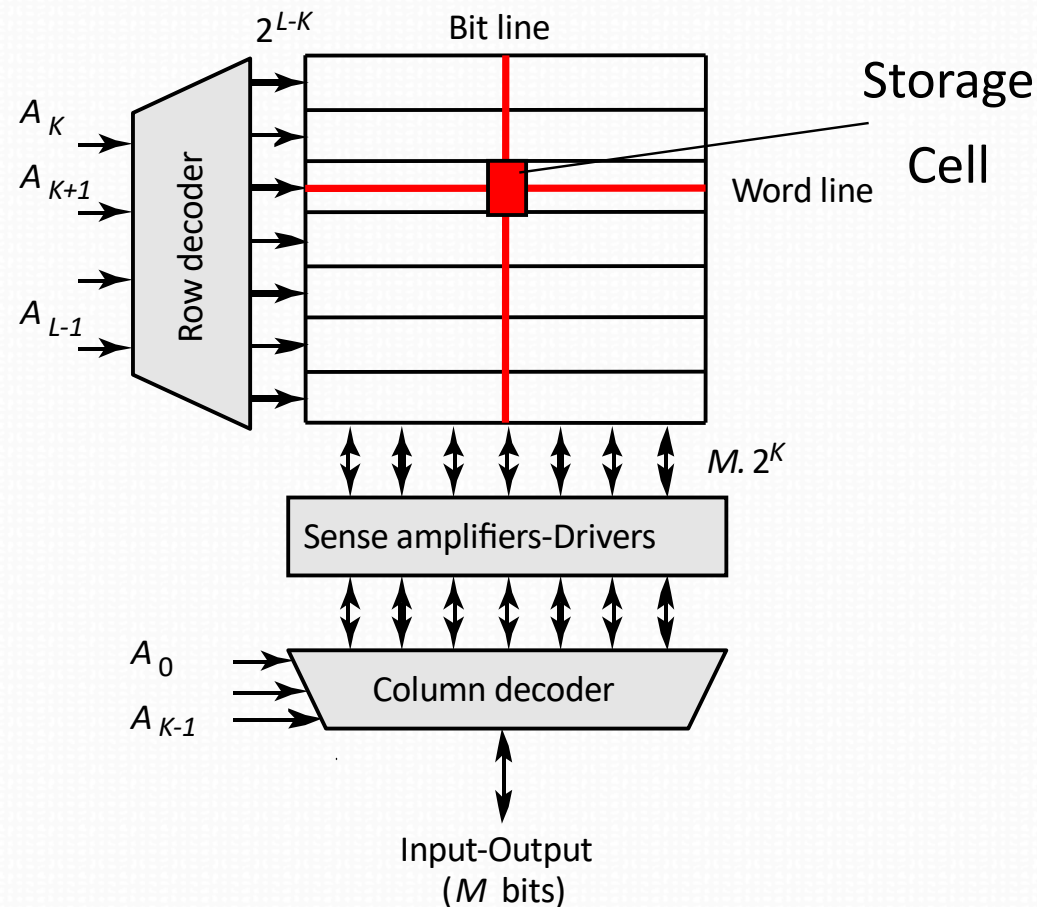
# Memory




- L2 Cache contains 4 Millions SRAM cells
  - Row/column of 2000 cells



# Outline

- The Fundamental Element: MOSFET Transistor
- Design of CMOS Cells: Combinatorial Logic
- Memory Cells
- Delay
- Power Consumption
- Synchronous Design
- Multicore: power and utilization walls
- Hardware accelerators

# Delay: Parasitic Elements

 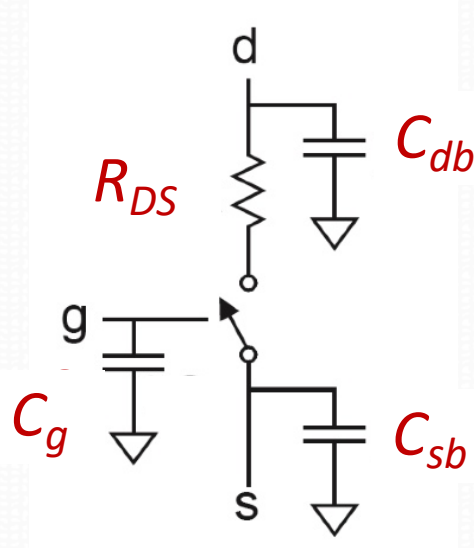 



- Drain-Source Resistance:  $R_{DS} = \frac{L}{W} \frac{1}{k(V_{dd} - V_t)}$
- Gate Capacitance:  $C_g = \frac{\epsilon W \cdot L}{t_{ox}} = W \cdot L \cdot C_{ox}$

$$\text{Delay} \propto R_{DS} \cdot C_g \propto \frac{L^2}{V_{dd} - V_t}$$



# Simplified Delay Model


CMOS Inverter

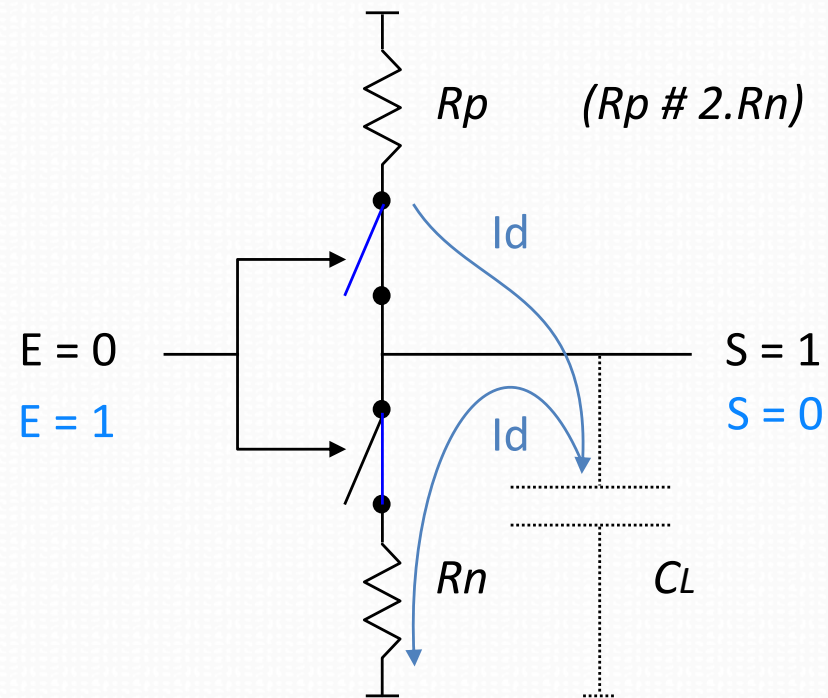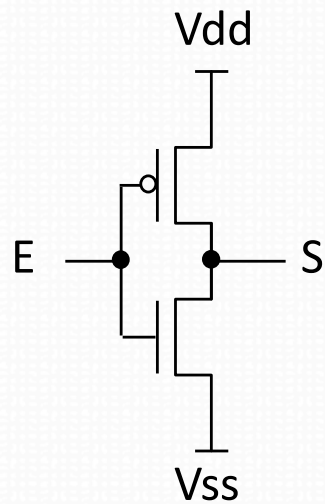

- Rising Output:  $t_{plh} = R_p.C_L$
- Falling Output:  $t_{phl} = R_n.C_L$

# Delay of Complex Gates


## k-input NAND

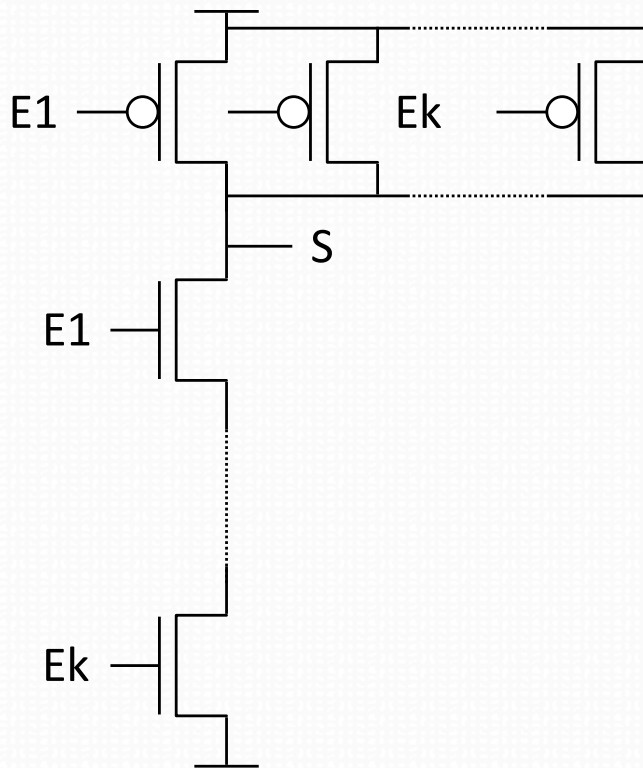

$$t_{pLH} = R_p \cdot C_L$$

$$t_{pHL} = k \cdot R_n \cdot C_L$$

## k-input NOR

 


$$t_{pLH} = k \cdot R_p \cdot C_L$$

$$t_{pHL} = R_n \cdot C_L$$


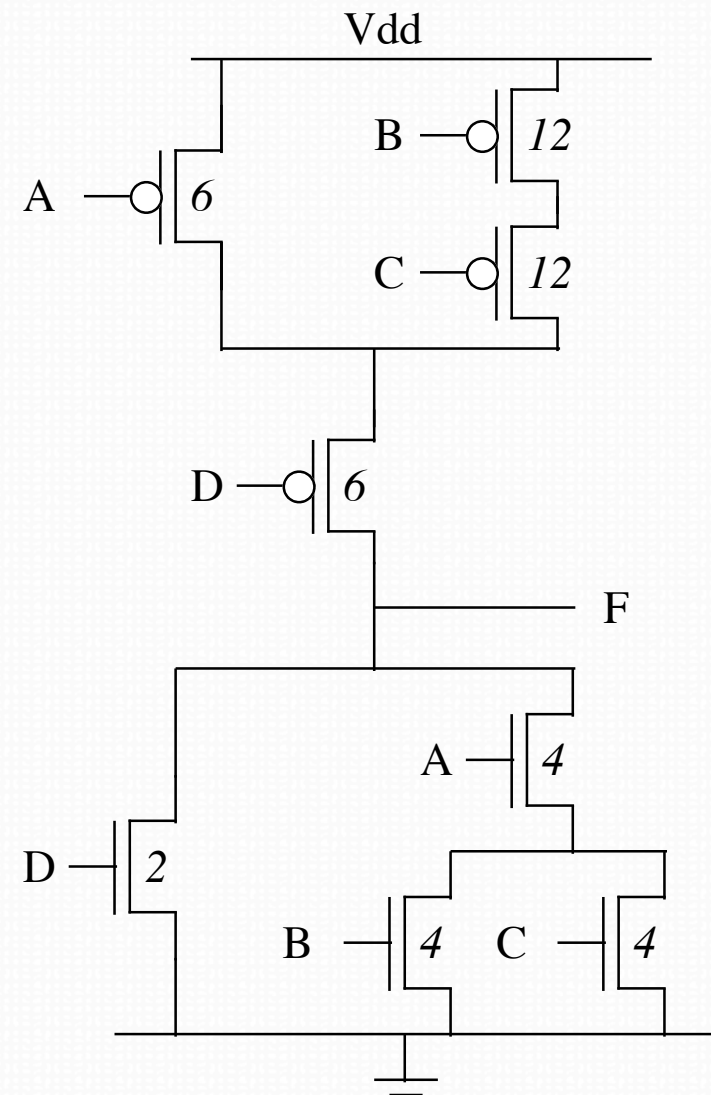
# Transistor Sizing

- $F = \overline{A \cdot (B + C) + D}$
- The art of **transistor sizing**
  - Equilibrate delay for  $0 \rightarrow 1$  and  $1 \rightarrow 0$  output transitions
  - Minimize cell area



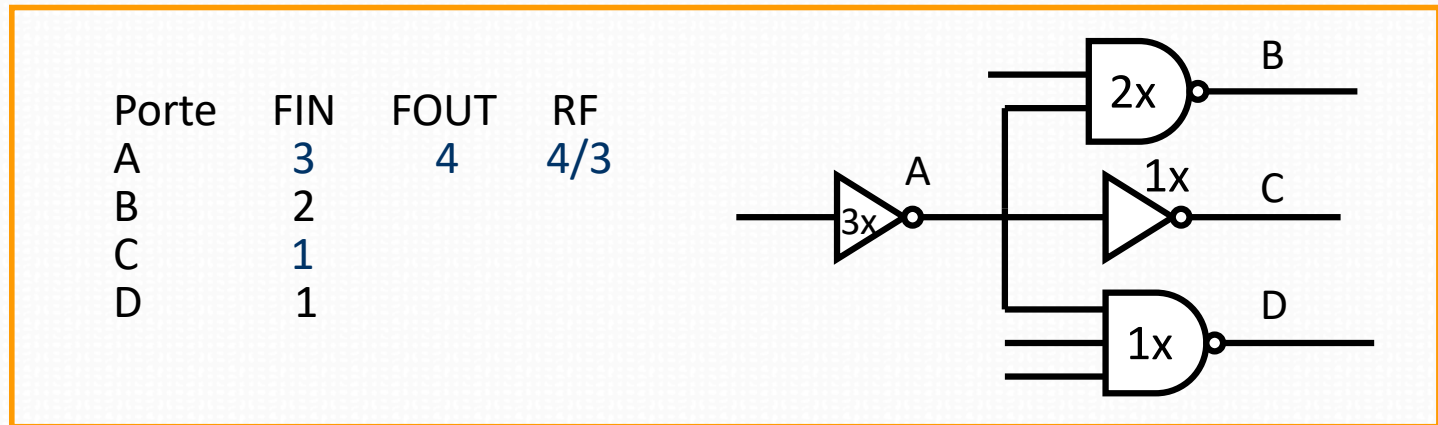 
# Logic-Level Delay Model

- Fan-In (or Drive): relative to size of transistors
  - Basic inverter is 1x
- Fan-Out: ratio between load capacitance and drive
- Relative Fan-Out (RF): ratio between fan-out and next-stage fan-in


 
# Logic-Level Delay Model

- $T_p = \text{transport delay} + \text{inertial delay} = TD + ID$
- $ID = RF \cdot UD$



$$T_p = TD + RF \cdot UD$$

UD: unit delay

# Outline

- The Fundamental Element: MOSFET Transistor
- Design of CMOS Cells: Combinatorial Logic
- Memory Cells
- Delay
- **Power Consumption**
- Synchronous Design
- Multicore: power and utilization walls
- Hardware accelerators


# Power and Energy Consumption

- Dynamic power
  - Charge and discharge of node capacitance

- Energy =  $C.V_{dd}^2$


- Power
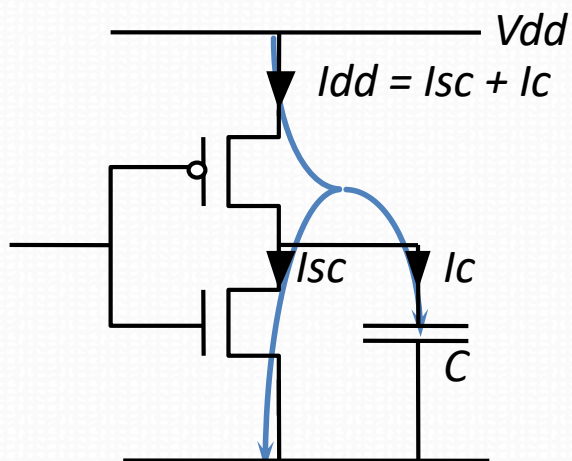
$$P_{dyn_i} = C.V_{dd}^2.f.Prob_{0 \rightarrow 1}$$



- Static power:  $P_s$ 
  - Sub-threshold and junction leakage current


$$P_{stat_i} = N.I_{off}.V_{dd}$$

 



# Power at Higher Level

- Propagating activity

 


$$P = \sum_i [\alpha_i \cdot f_i \cdot C_i \cdot V_{dd}^2 + I_{leak_i} \cdot V_{dd}]$$

# Activity


- Activity  $\alpha_i$  is the **probability** to have a  $0 \rightarrow 1$  transitions at the output of a gate
- Example: AND gate

–  $P_S = P(S=1) = P_A P_B$

–  $\alpha_i = P_S(1 - P_S)$


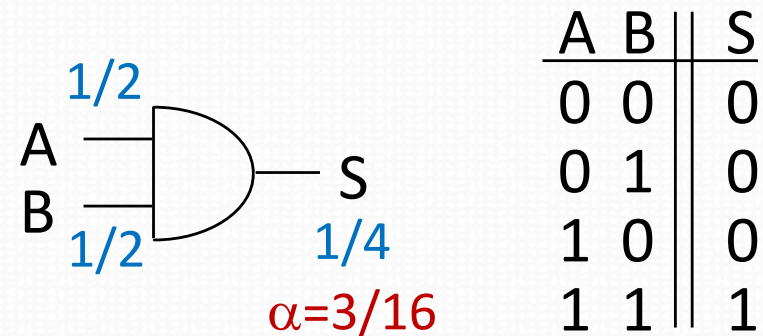


- Activity propagation

 


# Propagating Activity is not So Simple

- Conditional probabilities

  

 
- Glitches: gate delay
  - Significant in arithmetic


 
# Dynamic Power vs. Performance

- Decreasing Vdd reduces power **but** increases delay


$$P_{\text{dyn}_i} = \alpha_i \cdot f_{\text{clk}} \cdot C_i \cdot V_{\text{dd}}^2$$



$$\text{Delay} \propto \frac{1}{V_{\text{dd}} - V_t}$$

# Leakage vs. performance


- High performance

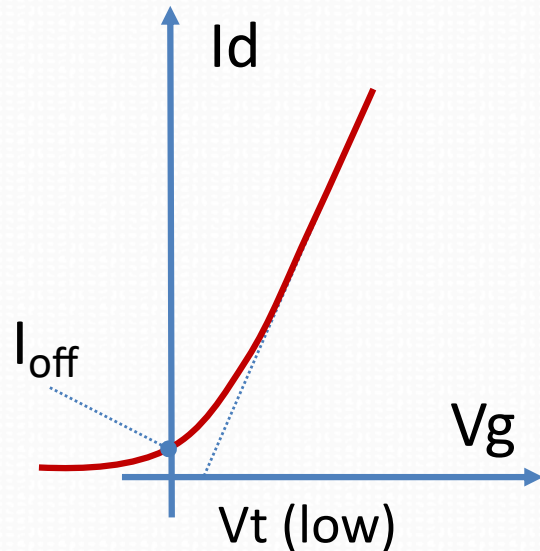

$$P_{stat_i} = N \cdot I_{off} \cdot V_{dd}$$

$$\text{Delay} \propto \frac{1}{V_{dd} - V_t}$$

- Low leakage

 


$I_{off}$ :

- Exponential in inverse of  $V_t$
- Exponential in temperature
- Linear in device count


# Minimum Energy per Operation

- Putting all together

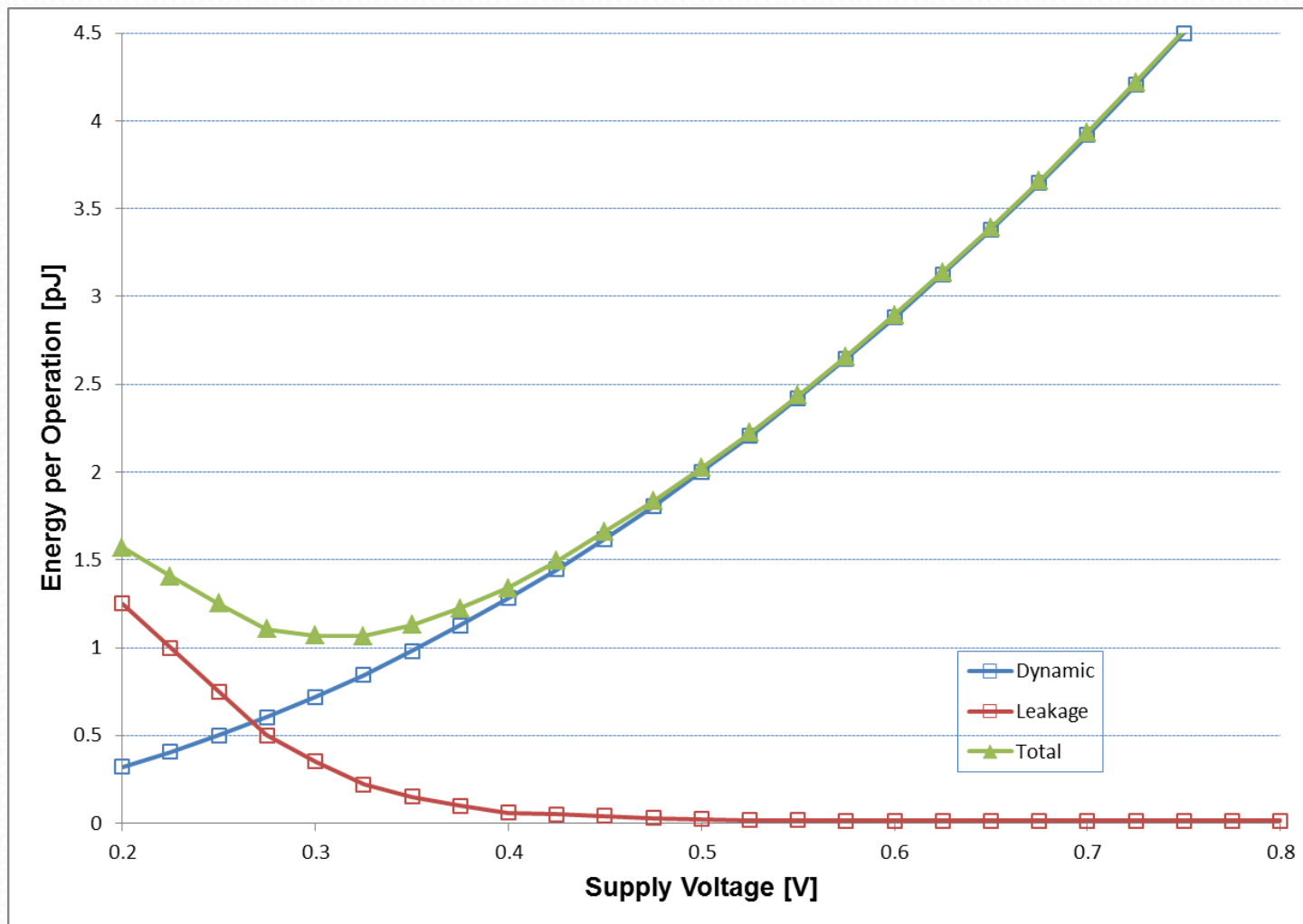
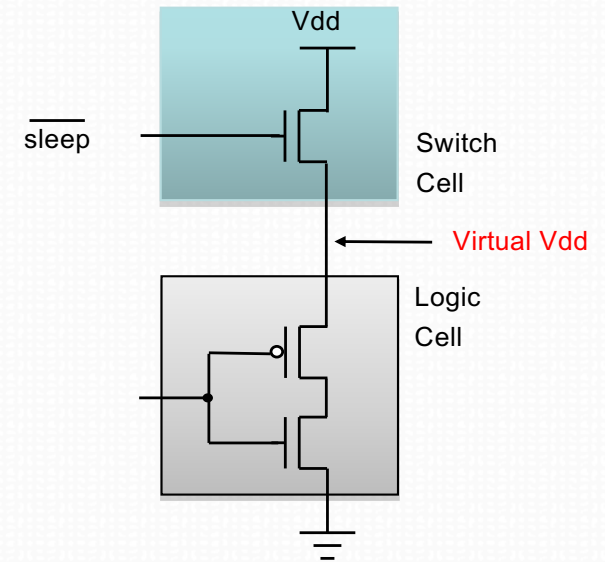
# Reducing Power


- Power gating, multi-Vt
- Clock gating
- Vdd scaling
  - Parallel, pipeline
- Activity reduction
  - Pre-computation, correlation, encoding
- Glitch Power Reduction




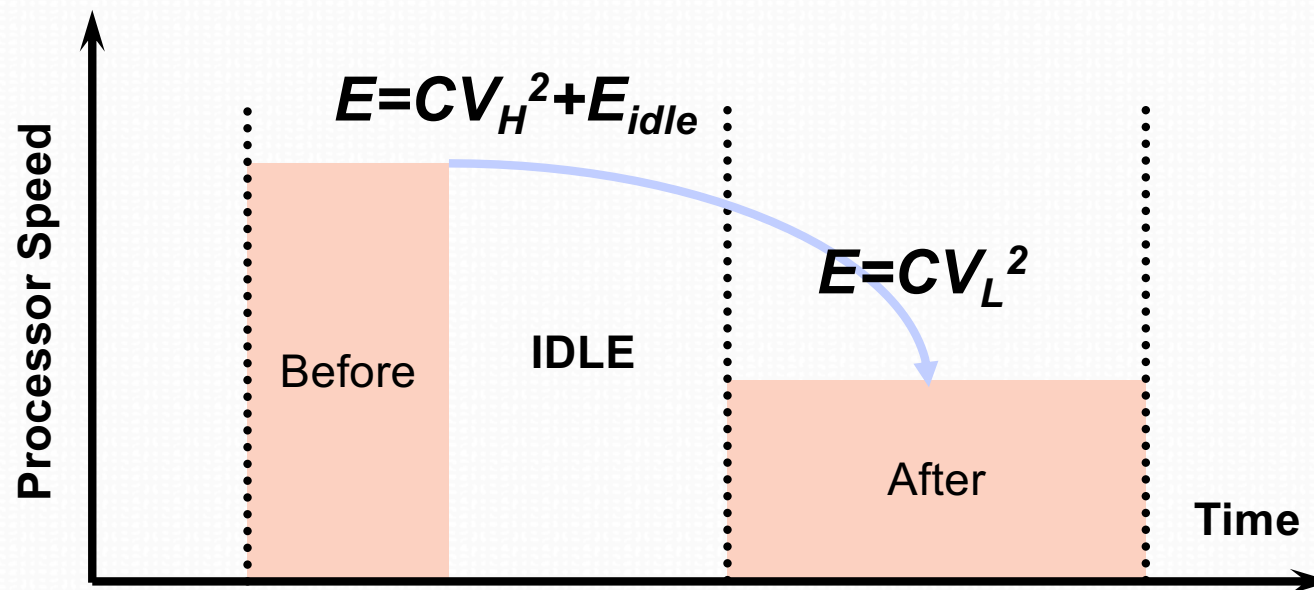
# Dynamic Power Management

- Dynamic Voltage and Frequency Scaling (DVFS)
- Reduce speed (clock freq.) and  $V_{dd}$  depending on processor activity



# Conclusion: Power in CMOS

$$P = \sum_i [\alpha_i \cdot f_i \cdot C_i \cdot V_{dd}^2 + I_{leak_i} \cdot V_{dd}]$$

$$P = \frac{\text{energy}}{\text{operation}} \times \text{rate} + \text{static power}$$


- Dynamic power
  - 40-70% today
  - Decreasing relatively
  - DVFS becomes more and more difficult
- Leakage power
  - 20-50 % today
  - Increasing rapidly
    - number of transistors
    - V<sub>dd</sub>/V<sub>t</sub> scaling
  - Critical for memory

# Outline

- The Fundamental Element: MOSFET Transistor
- Design of CMOS Cells: Combinatorial Logic
- Memory Cells
- Delay
- Power Consumption
- **Synchronous Design**
- Multicore: power and utilization walls
- Hardware accelerators

# Timing Parameters

- D Flip-Flop

 

- Setup Time: **T<sub>setup</sub>**

- amount of time the data at the synchronous input (D) must be stable **before** the active edge of clock


- Hold Time: **T<sub>hold</sub>**

- amount of time the data at the synchronous input (D) must be stable **after** the active edge of clock


- Propagation Time: **T<sub>p</sub>**

- amount of time for the data at the output (Q) to change **after** the active edge of clock

# Synchronous Circuits

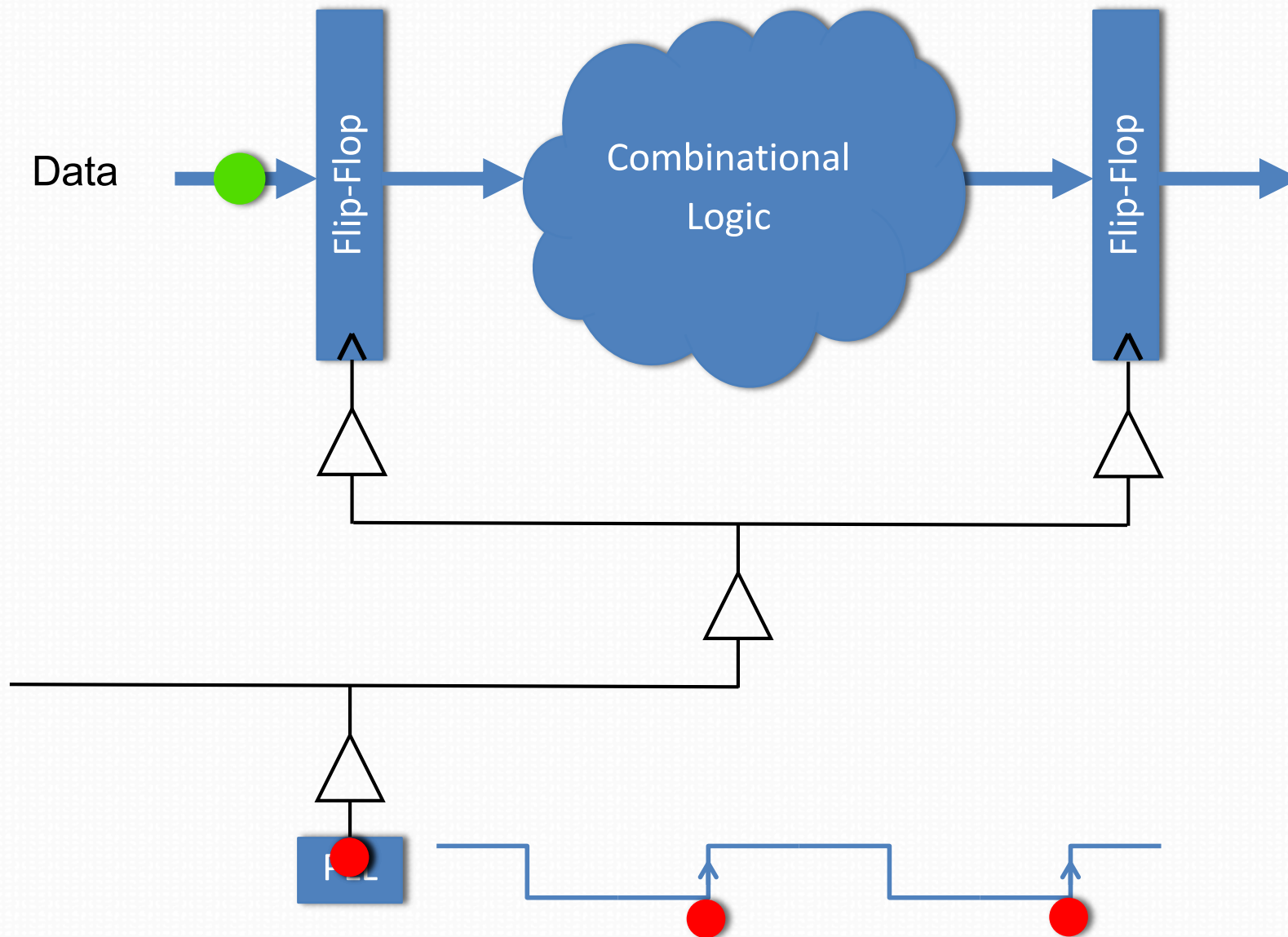

# Synchronous Circuits

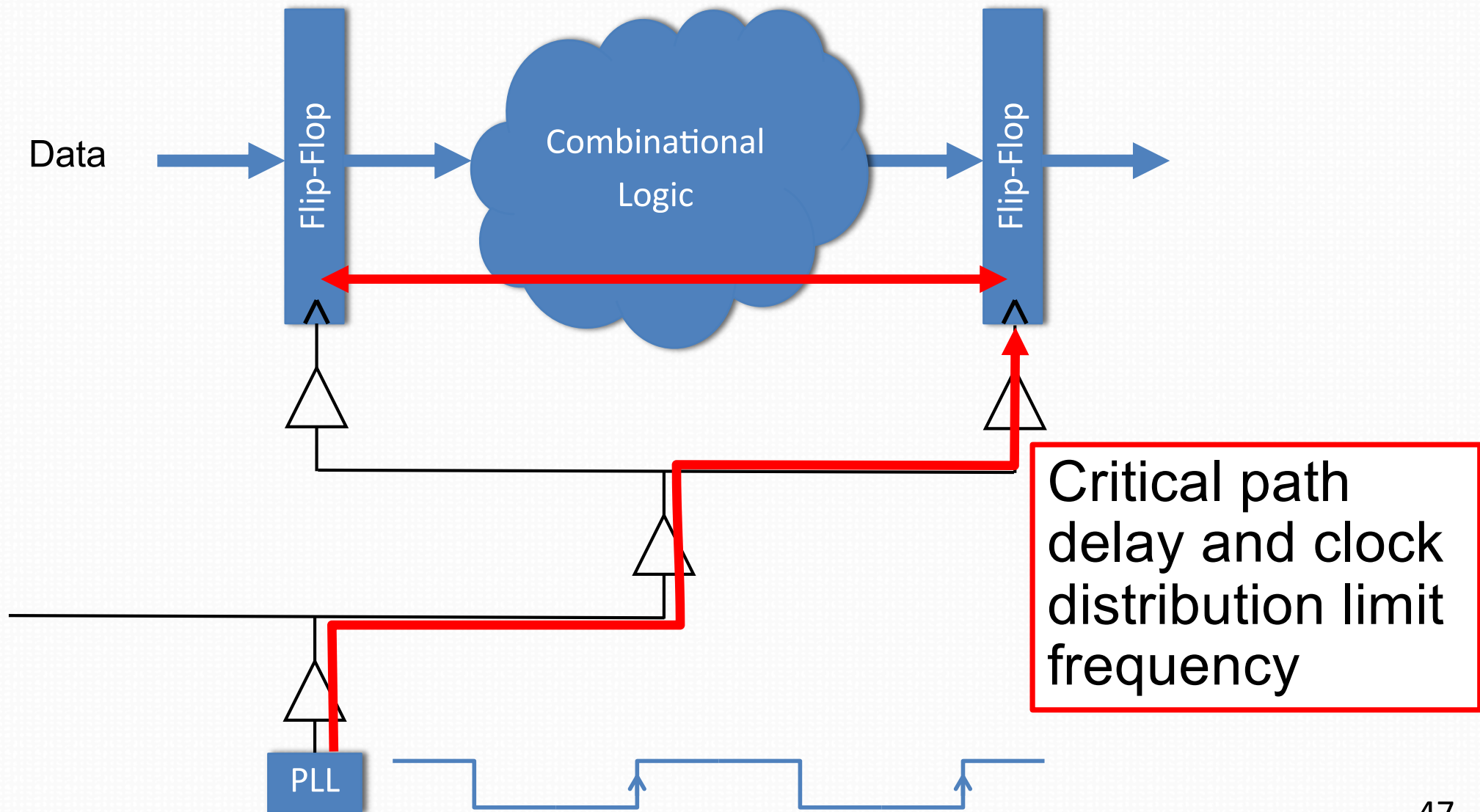



# Critical Path

- All circuits have a **maximal frequency**, which is given by finding its **critical path**
  - Data must be stable when sampled by the clock
- $T_{cp}$ : critical path delay of the logic

$$T_{cp} = \underset{\forall i}{MAX}(D_i), \text{ with } D_i \text{ Delay of path } i$$


- Maximal Frequency

$$F_{clk_{max}} = \frac{1}{T_{cp} + T_p + T_{setup}}$$

# Critical Path in Processor Pipelines


- A typical (yet simple) processor pipeline

Critical Path

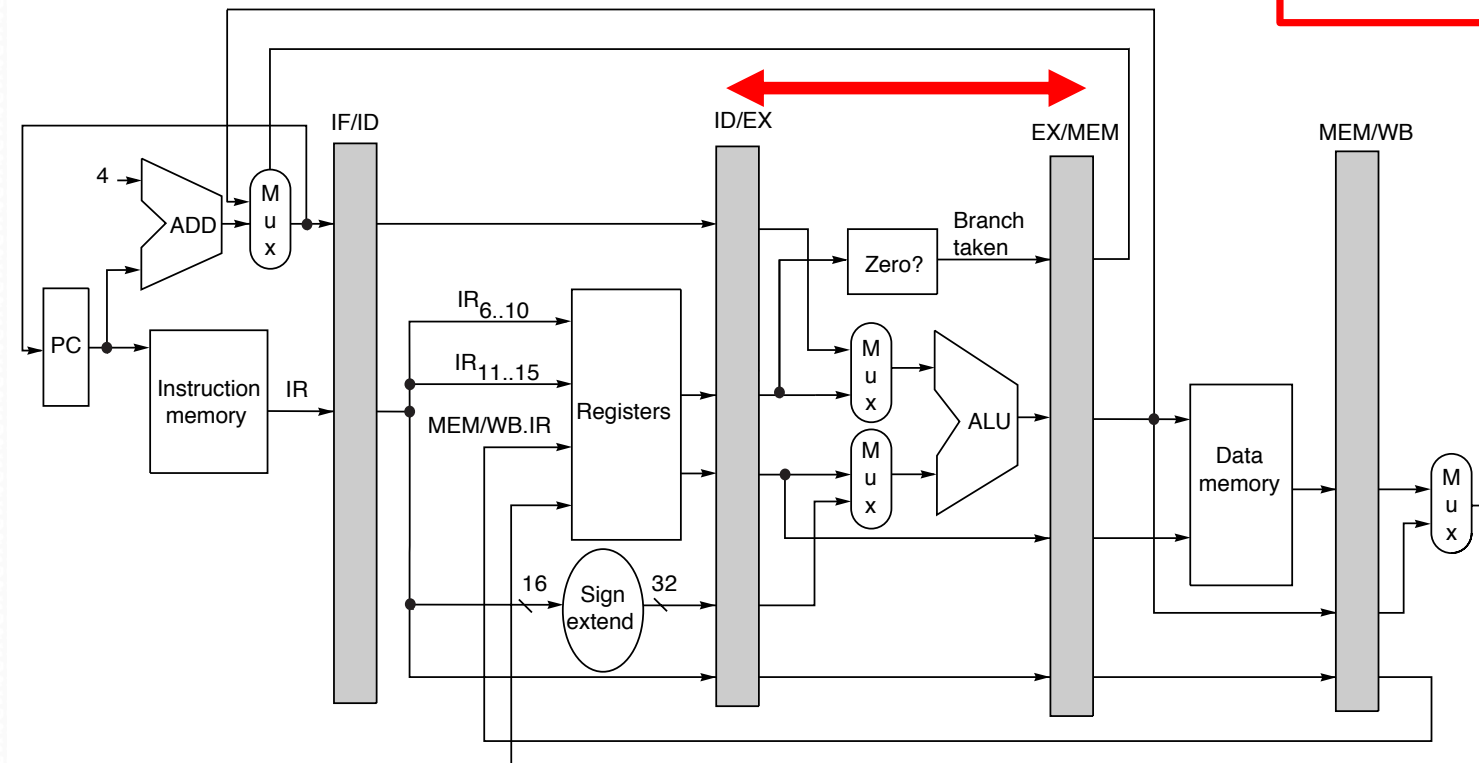
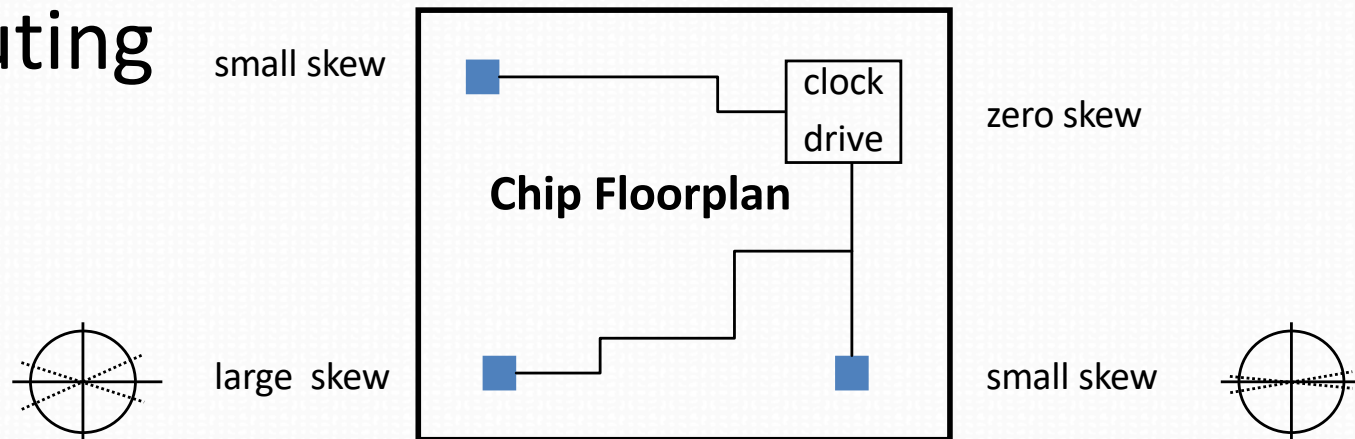
# Clock Skew

- Every FF receives the clock edge at a different time
- Clock routing



- Reduction of maximal frequency: 
$$Fe_{\max} = \frac{1}{T_{cc} + T_p + T_{setup} + \delta}$$



- Maximal skew for circuit operation: 
$$\delta < t_{p1} + \text{MIN}(t_{comb}) - t_{hold}$$

- Race between data and clock

  
# Clock Distribution

- Geometric buffering
- Tree-based

**H-tree:** constant skew in each block with equivalent number of flip-flops



**Buffering:** local reduction of skew

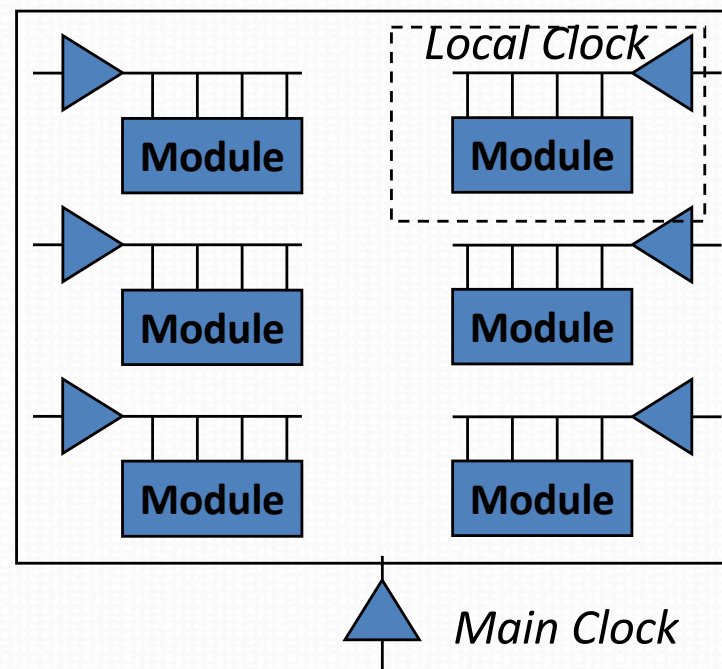


# Outline

- The Fundamental Element: MOSFET Transistor
- Design of CMOS Cells: Combinatorial Logic
- Memory Cells
- Delay
- Power Consumption
- Synchronous Design
- **Multicore: power and utilization walls**
- Hardware accelerators

# Inside (Simple) Processor Architecture
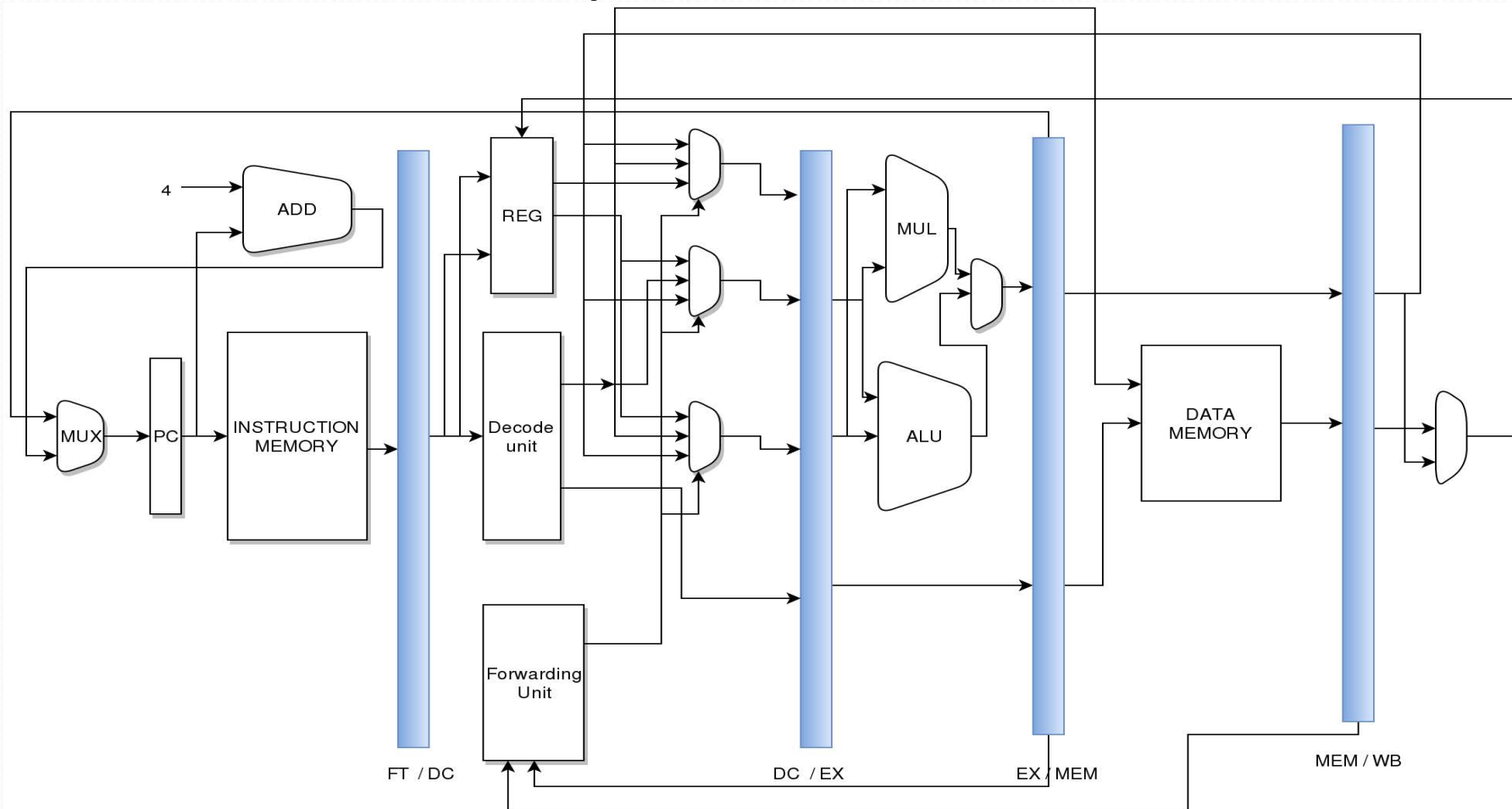
# Microarchitecture Pipeline


- Microarchitecture defines how instructions are executed (not unique)




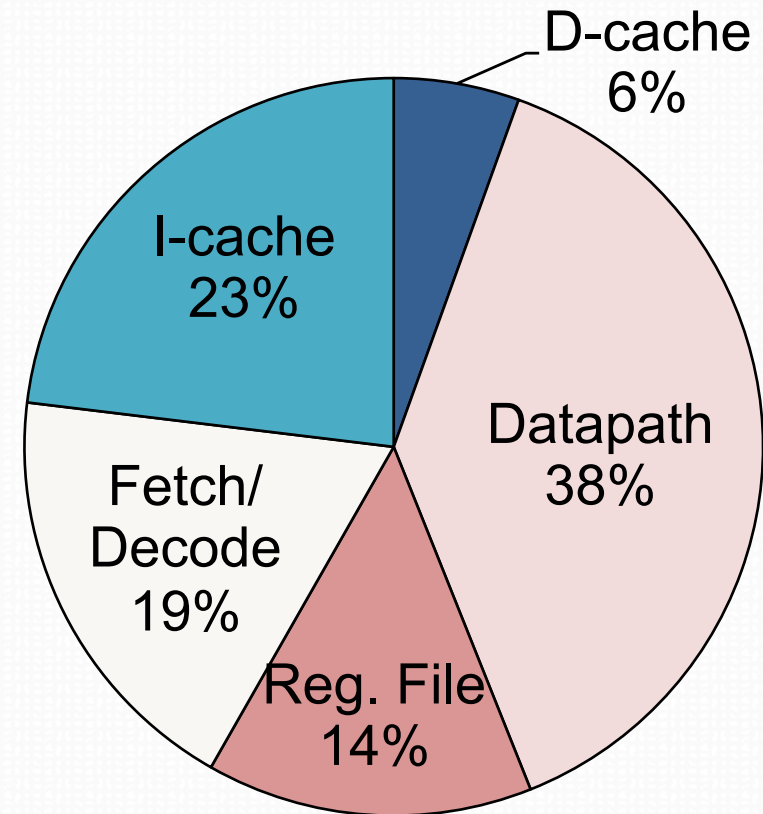
# Energy Cost in a Processor


- Operation:
  - 32-bit addition: 0.05pJ
  - 16-bit multiply: 0.25pJ
  - 64-bit FPU: 20pJ/op
- Instruction:
  - fetch, decode, read 2 operands from RF, execute, write back



MIPS Proc.  
91 pJ/instr.
 
# Achieving Higher Performance


- Pushing clock frequency...
- Branch/value prediction
- Cache memory
- In-core parallelism
  - Multiple FUs
  - Out of order execution
  - VLIW+good compilers



- Multiple cores on a single chip

Multicore: it's all a trick!  
Power and Utilization Walls

# And then came the "Power Wall"

 


Data partially collected by M. Horowitz, F. Labonte, O. Shacham, K. Olukotun, L. Hammond

Source: C. Batten, Cornell
 
# and the “Multicore Era”

- Increasing performance by increasing # of cores




–Source: C. Batten, Cornell




# Moving to multicore


- 1 core@2GHz@1.2V@1W

 


- 1 core@1GHz@0.8V@0.25W

 

- 2 cores@1GHz@0.8V@0.5W

 


- But... twice area (and not so simple)

 


- Advanced technology nodes?



# Technology Scaling

 


Intel's Xeon Chip

 



28 nm

  

20 nm

 


14 nm

  


## Classical (Dennard's) scaling

Device count	$S^2$
Device frequency	$S$
Capacitance, $V_{dd}$	$1/S$
Device power	$1/S^2$
<b>Utilization</b>	<b>1</b>

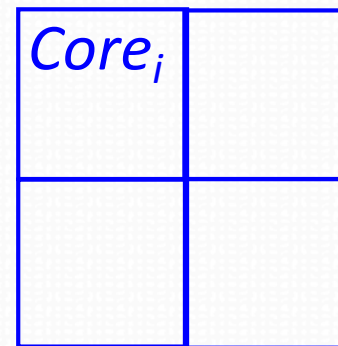

100W@f

 

50W@1.4.f





# End of Dennard's Scaling


- Energy efficiency is not scaling along with integration capacity

## Leakage limited scaling

Device count	$S^2$
Device frequency	$S$
Device power (cap)	$1/S$
Device power ( $V_{dd}$ )	$\sim 1$
Utilization	$1/S^2$

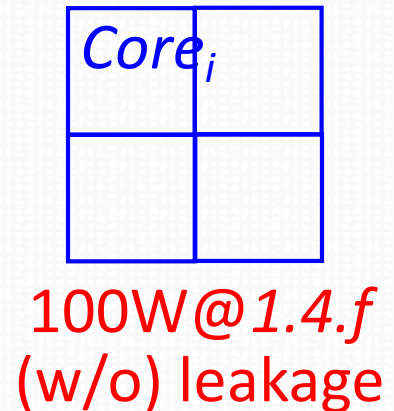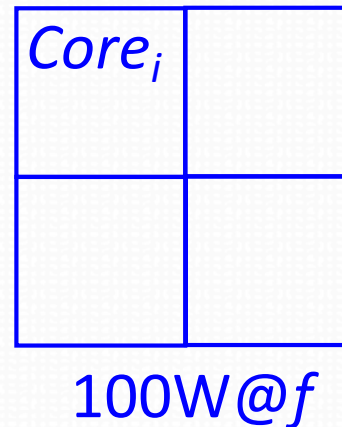


 - **Utilization Wall**: percentage of a chip that can switch at full frequency drops exponentially
- Replace dark cores with **specialized cores** (10-100x more energy efficient)



# End of Growth of Speed?


## 40 years of Processor Performance

 

Based on SPECintCPU. Source: John Hennessy and David Patterson, Computer Architecture: A Quantitative Approach, 6/e. 2018


# Pushing the Accelerator!

# What is a HW accelerator?

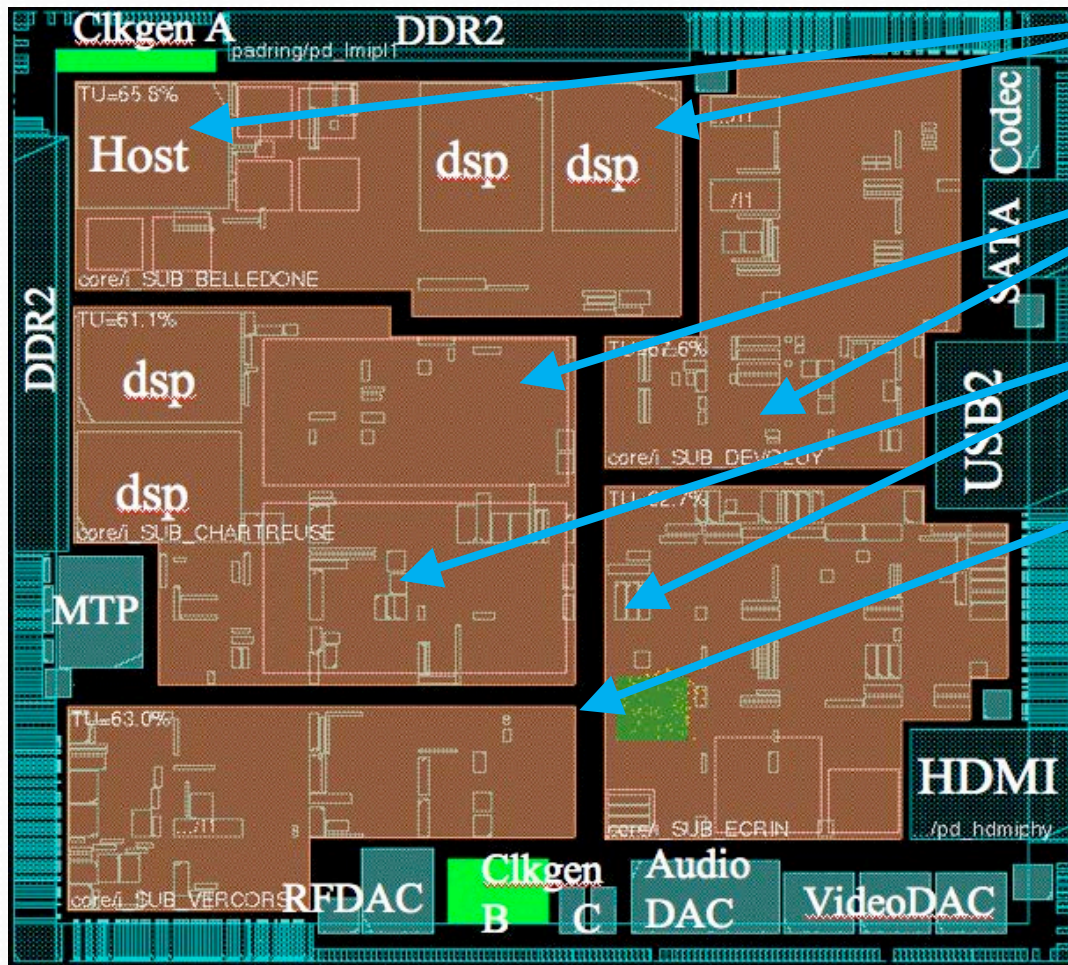


- 16 processors
- 38 HW blocks
- 140 memory blocks
- 5 Gbytes/s on-chip interconnection network

# Energy Savings in Specialized HW

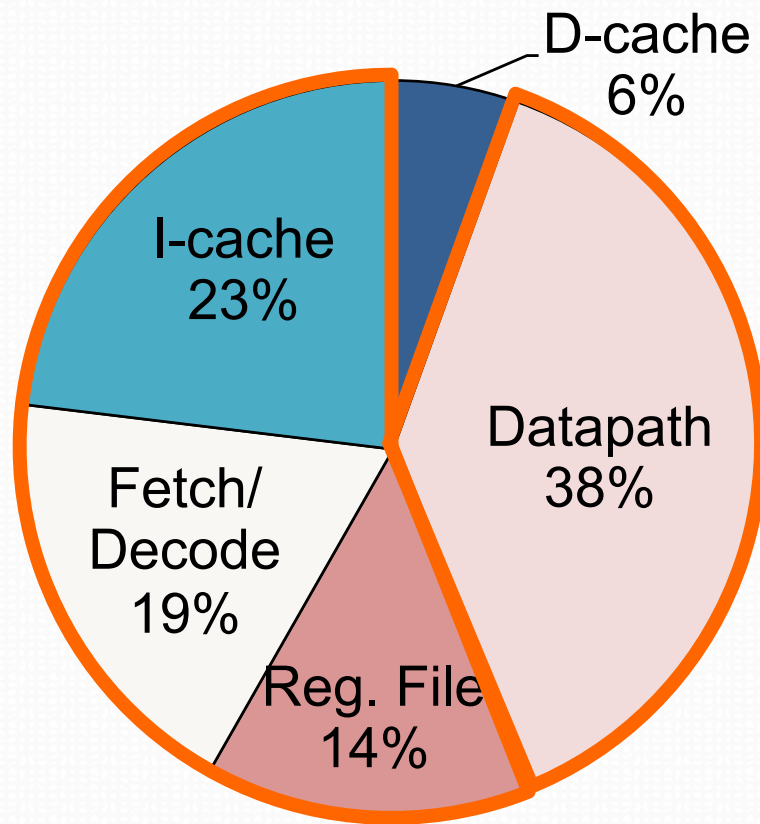

MIPS baseline  
91 pJ/instr.

 

Specialized core  
8 pJ/instr.



# An example: Bitcoin Mining



Type	Model	Mhash/s	Mhash/J	Power (W)
GPP	Intel Xeon X5355 (dual)	22.76	0.09	120
GPP	ARMCortex-A9	0.57	1.14	1.5
GPP	Intel Core i7 3930k	66.6	0.51	130
GPU	AMD 7970x3	2050	2.41	850
GPU	Nvidia GTX460	158	0.66	240
ASIC	AntMiner S1	180.000	500	360
ASIC	AntMiner S5	1.155.000	1957	590
FPGA	Bitcoin Dominator X5000	100	14.7	6.8
FPGA	Butterflylabs Mini Rig	25.200	20.16	1250



BITCOIN MINER

# Making ANN Inference more Efficient

- Main motivation: AlphaGo consumes around 250,000 Watts!
- Bring Logic and Memory closer
- Compute less precisely

## Tensor Processing Unit

ASIC for TensorFlow  
Designed by Google  
10x better perf / watt  
latency and efficiency  
bit quantization





- Google Tensor Processing Units (TPU)
  - Computations close to memory
  - 8 bit operations

# Reconfigurable Hardware Accelerators




# Field Programmable Gate Array (FPGA)

 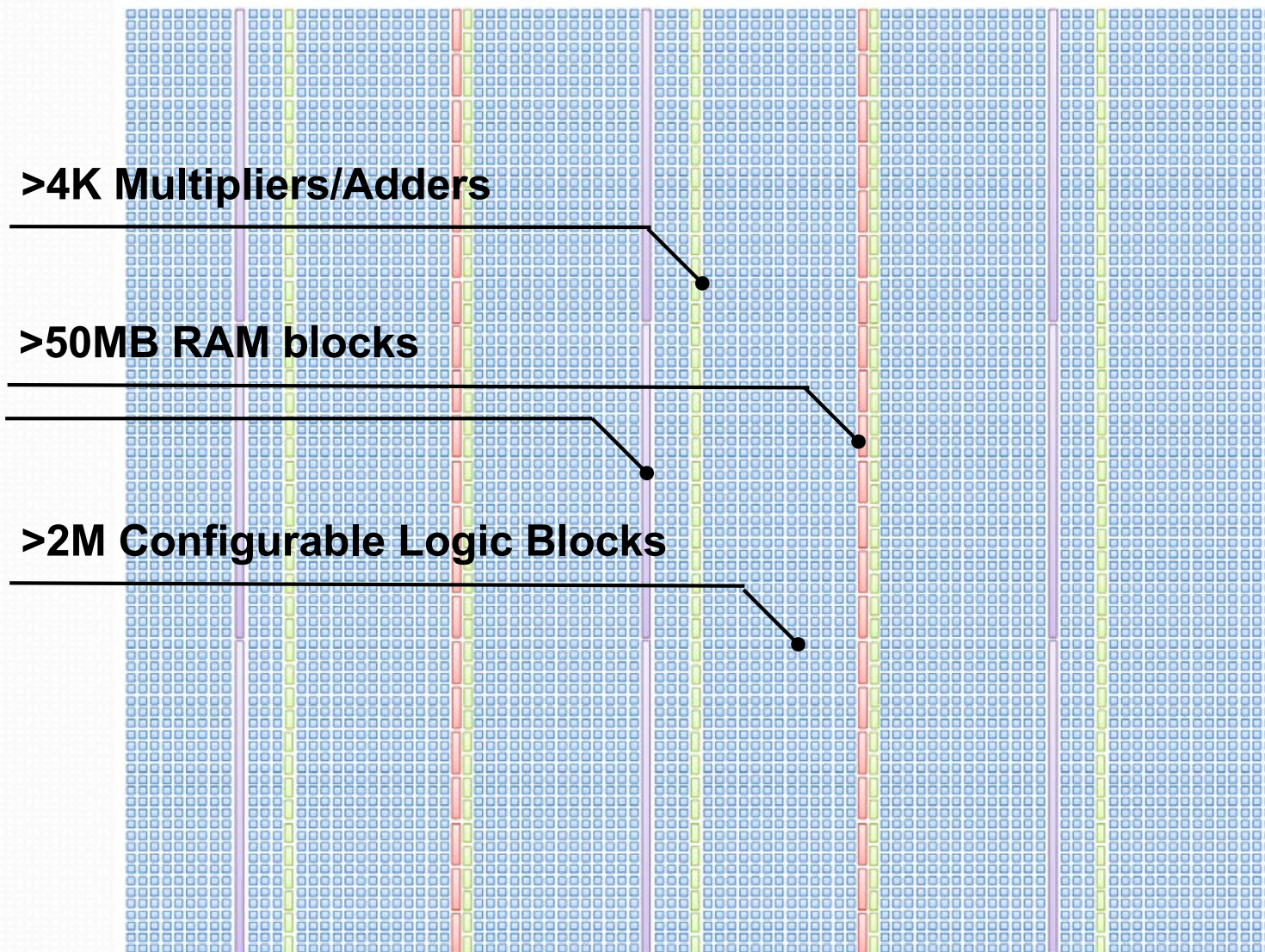




# Field Programmable Gate Array (FPGA)

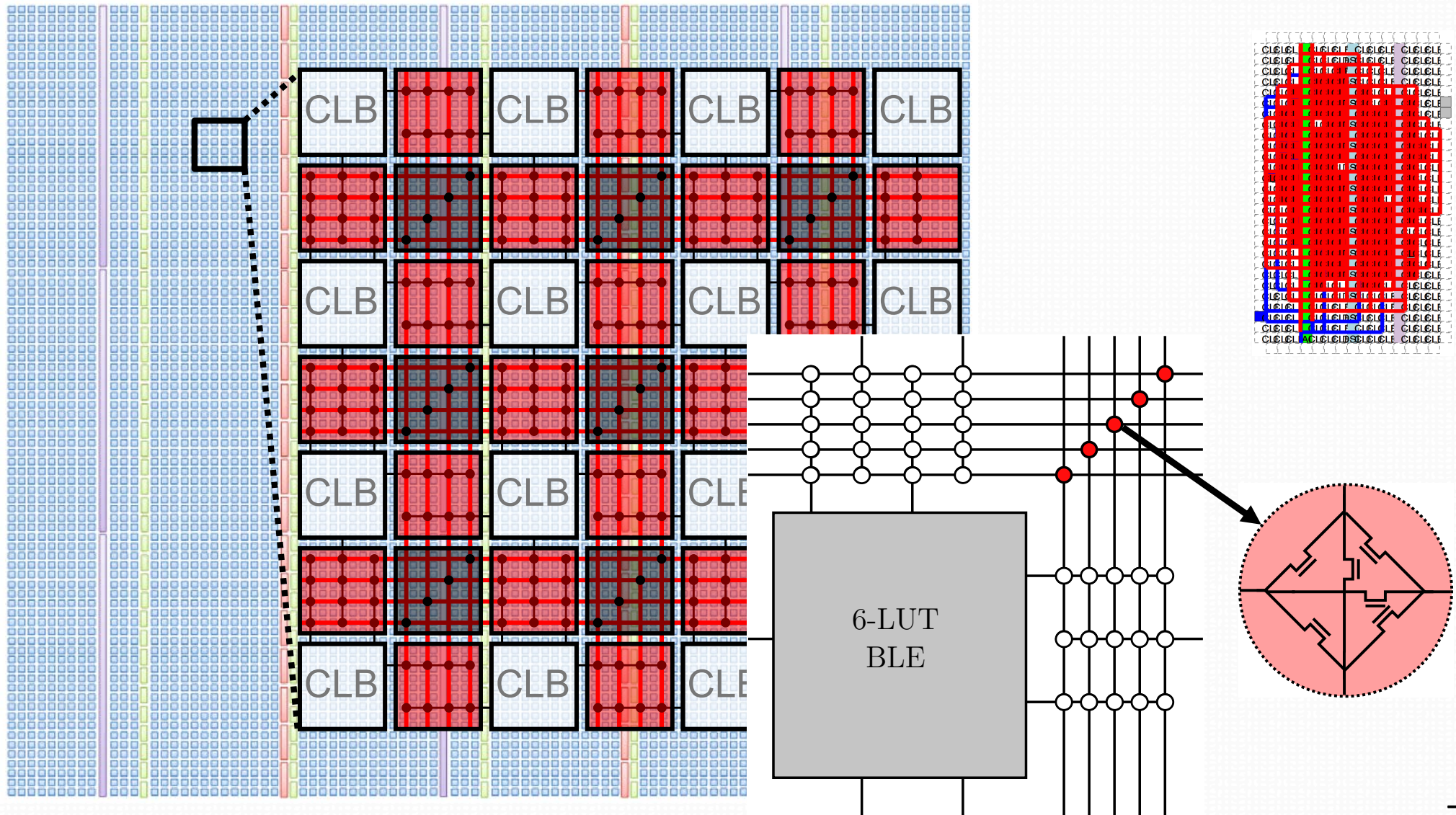




# The Program is the Configuration

 


(a) abs

 


(b) calcNeighbor

# The Program is the Configuration

 


(a) Crc16

 


(b) calcNeighbor
 
# Space-Time Computation

```
for(i=1; i<length; i++) {  
    if (max < T[i]) {  
        max = T[i];  
    }  
}
```



 
```
for(i=1; i<N; i++) {  
    for(j=1; j<M; j++) {  
        y[i][j]+=x[i][j]*h[j][i]  
    }  
}
```




 
# FPGA Acceleration

- FPGAs can run multiple tasks in parallel



FPGA accelerators  
for HPC/Cloud

- Towards heterogeneous multicores

# Amazon AWS EC2 F1



## HARDWARE DEVELOPMENT KIT




Write your FPGA code with the FPGA Hardware Development Kit and FPGA Developer AMI

## CUSTOM LOGIC



Register compiled code as Amazon FPGA Image (AFI)

## AMAZON FPGA IMAGE (AFI)

 

Attach your AFI to an F1 Instance

## AWS MARKETPLACE




Associate your AFI with an AMI and offer on the AWS Marketplace



Attach your AFI to an F1 Instance

## F1 INSTANCE

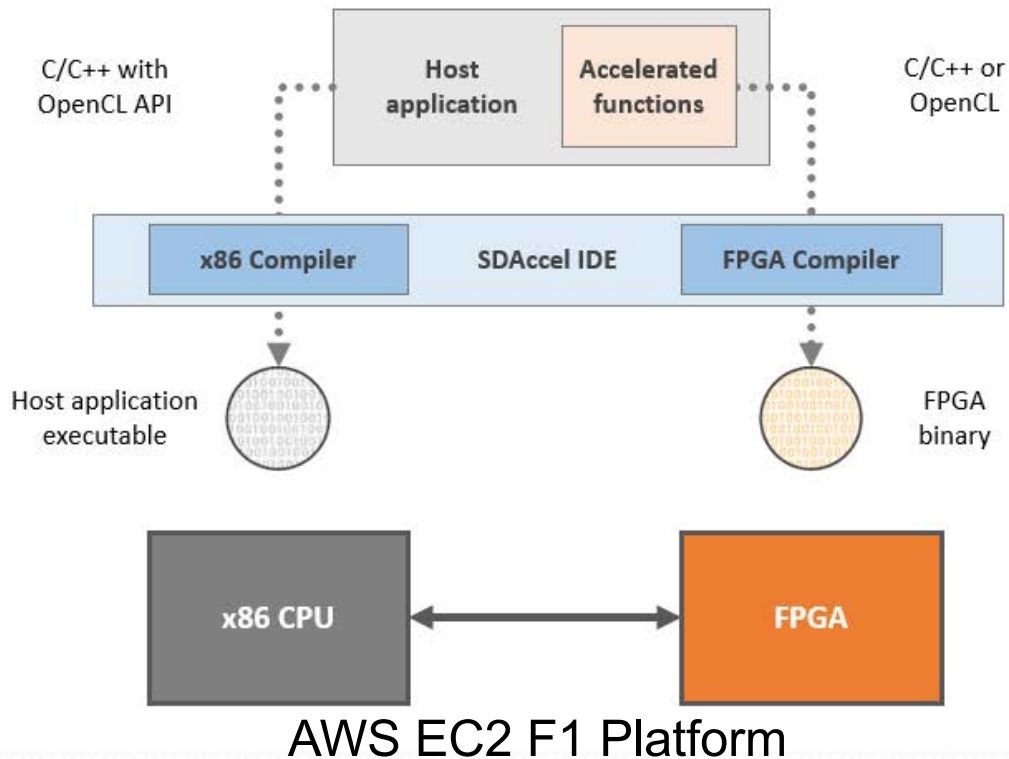

Instance Size	FPGAs	DDR-4 (GiB)	vCPUs	Instance Memory (GiB)	NVMe Instance Storage (GB)	Network Bandwidth
f1.2xlarge	1	4 x 16	8	122	1 x 470	Up to 10 Gbps
f1.16xlarge	8	32 x 16	64	976	4 x 940	25 Gbps

- Up to 8 Xilinx UltraScale+ FPGA devices in a single EC2/F1 instance

# Time has Come for Specialization

- Microsoft Unveils Catapult to Accelerate Bing
  - One FPGA per blade
  - $6 \times 8$  2-D torus topology
  - High-end Stratix V FPGAs
- Running Bing Kernels for feature extraction and machine learning
- Increase **ranking throughput by 95%** at comparable latency to software-only
- Increase power consumption by 10%
- Increase total cost of ownership by less than 30%






# Conclusions


- A **not too** deep dive into processors?
- Transistors, logic gates, registers and memory
- Delay and maximal frequency
- **Power** is data dependent and dominated by data transfers
- Energy efficiency **is no more** scaling along with integration density
- Efficiency of hardware **specialization**
 
# Conclusions

- Energy consumption
  - True in embedded
  - True in HPC, n




 
- End of Moore's law...
- Multicores but utilization wall
  - Percentage of a chip that can switch at full frequency drops exponentially



Dark Silicon
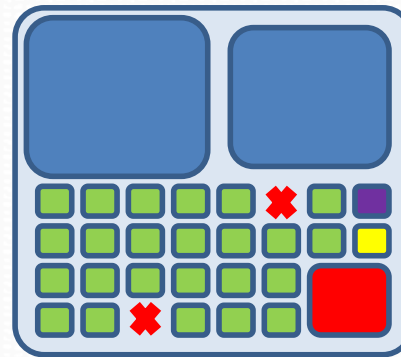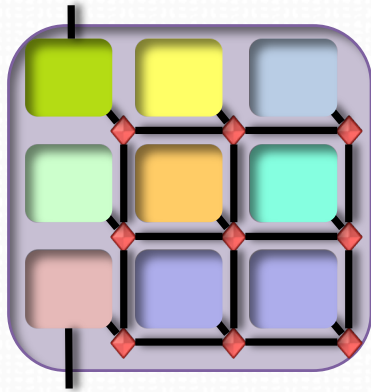
# What's next?


- Dark Silicon is also an opportunity
  - **Heterogeneous** manycore architectures




- Efficiency of hardware **specialization**
  - Domain-specific architectures and languages
- Computing **just** right
  - @design-time or @run- time
 
# What's next?


- **Emerging devices**
- Cells, brain, neurons have “analog” behavior
- And compute with very low precision
- Making neuromorphic computing more efficient



*Phase  
Change  
Memory*

 

 *Memristors,  
Oxide  
Resistive  
Memory*



***Spin  
Torque  
Magnetic  
Memory***